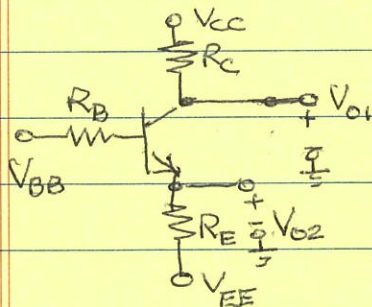



TEXT PROBLEMS: 4.20, 4.34, 4.37

PROBLEM AParameters: $\beta = 100$, $R_C = 0.5 \text{ k}\Omega$, $R_E = 1.0 \text{ k}\Omega$ $R_B = 44 \text{ k}\Omega$, $V_{CC} = +15 \text{ V}$, $V_{EE} = -15 \text{ V}$

$$V_{BB} = -8 \text{ V}$$


1. Determine V_{O1} and V_{O2}
2. What new value of R_C makes $V_{O1} = 0$?
3. What new value of R_C makes $V_{O2} = 0$?

If one of these is not possible, why not?

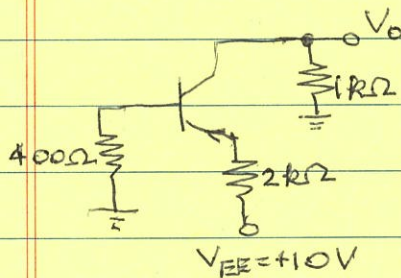PROBLEM B

1. $\beta = 150$, determine I_C and V_{CE} .
2. Repeat (1) for $\beta = 50$

NOTE: the BJT is a pnp.

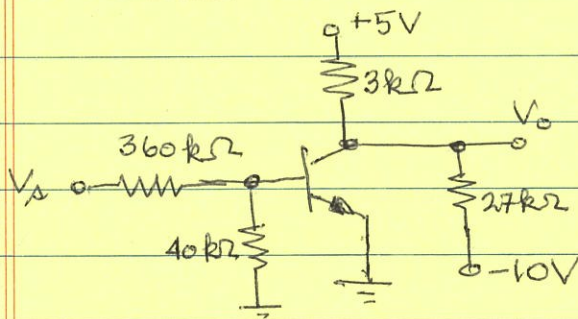PROBLEM C

Given $\beta = 150$ and the BJT has negligible saturation current, sketch the transfer characteristic V_O vs. V_S for $-10 \text{ V} \leq V_S \leq +10 \text{ V}$. Carefully label all critical ordinate and abscissa values.