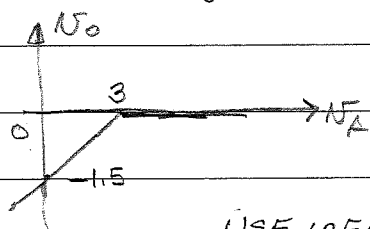


Text Problems : 3.15, 3.53, 3.58, 3.60

### PROBLEM A

The voltage transfer characteristic  $V_o$  vs.  $V_A$  is




USE IDEAL DIODES Transfer characteristic shown.

1. Sketch  $V_o$  if  $V_A(t) = 2 + 3 \sin \omega t$

2. Design a simple diode circuit that results in the voltage

### PROBLEM B

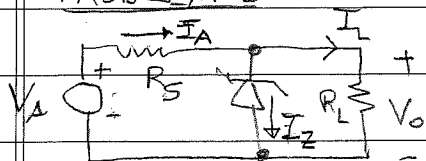

In the circuit shown a 5V-Zener diode with  $R_Z = 0$  provides regulation for  $50 \text{ mA} \leq I_A \leq 1 \text{ A}$

$R_S = 4.75$  and  $V_A$  varies between 7.5V and 10V.

Find the range of  $I_L$  for which regulation is achieved.

### PROBLEM C

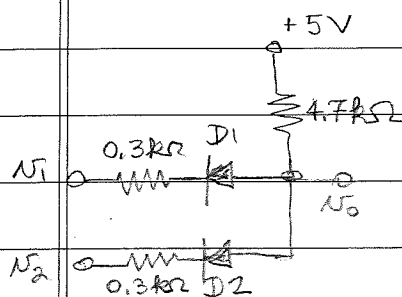


Fig. I

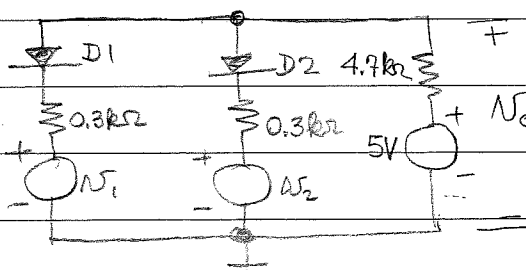


Fig. II

Figs. I and II are identical

The diodes in the circuit shown turn on with  $V_D = 0.6 \text{ V}$

Find  $V_o$  for a)  $V_1 = V_2 = 5 \text{ V}$ ; b)  $V_1 = 5 \text{ V}$ ,  $V_2 = 0$ ;

c)  $V_1 = 0$ ,  $V_2 = 5 \text{ V}$  and d)  $V_1 = V_2 = 0$