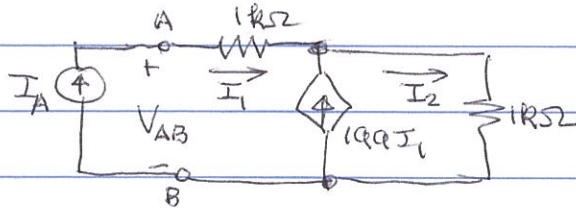


PROBLEM 1


Equivalent resistance is  $R_{AB} = V_{AB}/I_A$ . Apply a current source  $I_A$  and measure  $V_{AB}$



$$I_1 = I_A \quad I_2 = I_1 + 100I_1 = 200I_1 = 200I_A$$

$$V_{AB} = 1k\Omega \times I_A + 1k\Omega \times 200I_A$$

$$R_{AB} = \frac{V_{AB}}{I_A} = 1k\Omega + 200k\Omega = 201k\Omega$$

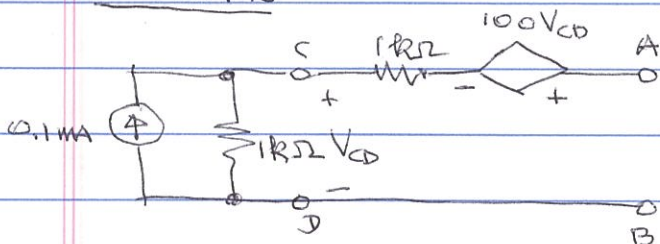PROBLEM 2

$V_{TH} = V_{AB}$  when A-B open-circuited.

No current exists from C to A


$$\therefore V_{CD} = 0.1mA \times 1k\Omega = 0.1V$$

$$V_{AB} = \frac{V_{AC}}{100 \times 0.1} + \frac{V_{CD}}{100} = V_{TH} = 10.1V$$

To find  $R_{TH}$  we can either find  $I_{sc}$  ( $I_{sc} = I_{AB}$  when A-B short-circuited) and  $R_{TH} = V_{TH}/I_{sc}$

OR suppress 0.1mA and apply a current  $I_A$  and measure  $V_{AB}$  as in Problem 1.

First find  $I_{sc}$ . Convert 0.1mA || 1kΩ to 0.1V in series with 1kΩ as shown

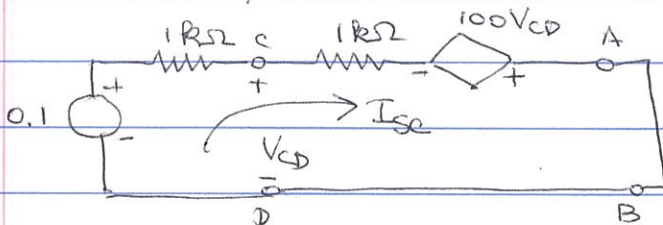

$$KVL: -0.1 + I_{sc}(1k + 1k) - 100V_{CD} = 0$$

$$V_{CD} = -I_{sc}(1k) + 0.1$$

$$\therefore -0.1 + I_{sc}(2k) - 100(-1kI_{sc} + 0.1) = 0$$

$$\text{and } 102k I_{sc} = 10.1 \quad \text{and } I_{sc} = 10.1/102k$$


$$R_{TH} = 10.1 / (10.1/102k) \text{ and } R_{TH} = 102k\Omega$$





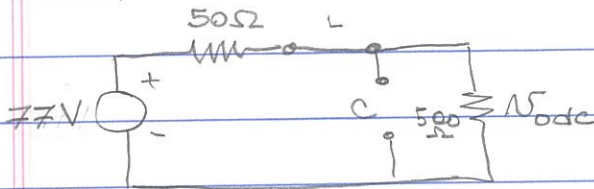PROBLEM 4

With two excitations, one dc and one ac, we must use superposition. For the dc excitation, the circuit is




Recall that in the dc steady-state inductances are short circuits and capacitances are open circuits

The circuit is a simple voltage divider so

$$V_{0dc} = \frac{500}{50+500} \times 77 \text{ and } V_{0dc} = 70V$$

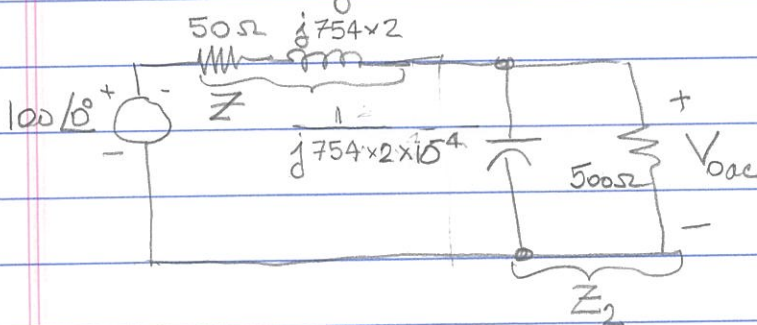For the ac circuit we use phasor analysis in which  $L$  becomes  $j\omega L$  and  $C$  becomes  $1/j\omega C$ . The circuit is



$$Z_1 = 50 + j1508$$

$$Z_2 = 500 \parallel \left( \frac{1}{j754 \times 2 \times 10^{-4}} \right)$$


$$Z_2 = 500 \parallel -j6.33 = 6.63 \angle -89.24^\circ$$

$$= 0.088 - j6.63$$

$$V_{0ac} = \frac{6.63 \angle -89.24^\circ \times 100}{50 + j1508 + 0.088 - j6.63} = \frac{663 \angle -89.24^\circ}{1502 \angle 88.09^\circ} = 0.441 \angle -177.3^\circ$$


$$\therefore V_{0ac} = 0.441 \cos(754t - 177.3^\circ)$$

$$V_0(t) = V_{0dc} + V_{0ac} = 70 + 0.441 \cos(754t - 177.3^\circ)$$

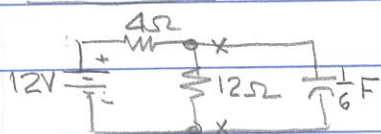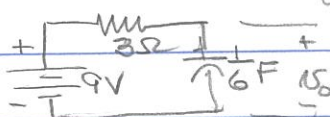PROBLEM 5

Circuit for  $t \geq 0$

Get Thévenin equivalent to the left of  $x-x$



$$R_{TH} = 4 \parallel 12 = 3\Omega$$

$$V_{TH} = \frac{12}{12+4} \times 12 = 9V$$


We know  $V_0$  starts at zero and charges to 9V with a time constant  $= 3 \times \frac{1}{6}$

$$\therefore V_0(t) = 9(1 - e^{-t/2}) = 9(1 - e^{-2t})$$
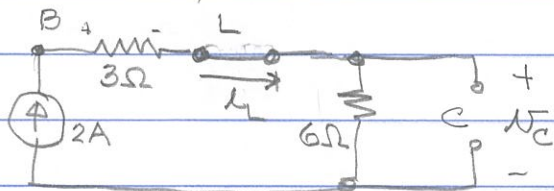
## PROBLEM 6


The key to this problem are the continuity relations for inductance current and capacitance voltage. These are that the current in an inductance and the voltage across a capacitance cannot change instantaneously. Thus, a change in excitation or circuit configuration at  $t=T$  requires  $i_L(T^+) = i_L(T^-)$  and  $v_C(T^+) = v_C(T^-)$  where  $T^-$  is the instant before and  $T^+$  is the instant just after the change occurs.

At  $t=0^-$ , the circuit is in the dc steady state and is



Thus,  $i_L(0^-) = 2A$  and  
 $v_C(0^-) = 6 \times 2 = +12V$

At  $t=0^+$ , the circuit becomes

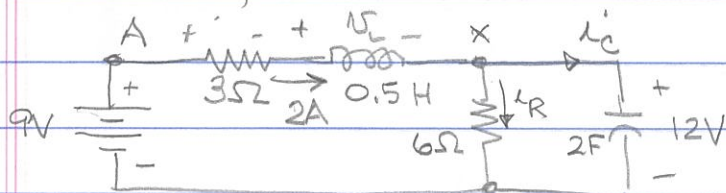

$$\begin{aligned} i_L(0^+) &= i_L(0^-) = 2A \\ v_C(0^+) &= v_C(0^-) = 12V \end{aligned}$$

$i_R = 12/6 = 2$  and KCL @ X gives

$$-2 + i_R + i_C = 0 \text{ and } i_C = 2 - 2 = 0$$

KVL requires  $-9 + 2 \times 3 + v_L + 12 = 0$  and  $v_L(0^+) = -9V$