

Text Problems: 2.10, 2.18, 2.23 a (only do a).

### Problem A

1. Design a non-inverting amplifier using an "ideal" Op-amp. The total resistance used must not exceed  $40k\Omega$  and the gain ( $|A_{v}| = 20$ )
2. Repeat (1) for an inverting stage.

### Problem B

1. An Op-amp has the following open-loop gain

$$A_{OL}(j\omega) = \frac{A_{OL}(0)}{1 + j\omega/\omega_R} \quad \text{where } A_{OL}(0) = 2 \times 10^5 \text{ and } \omega_R = 60 \text{ rad/s}$$

For the amplifier in A1, what is the bandwidth?

2. Two identical stages described above are cascaded. What is the new gain-bandwidth product of the cascade? What is the amplifier's bandwidth?