
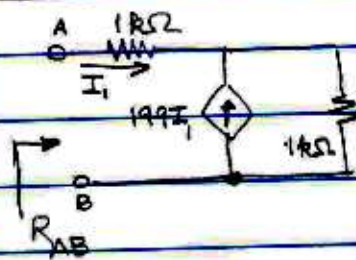


PROBLEM 1


Evaluate R_{AB}

PROBLEM 2

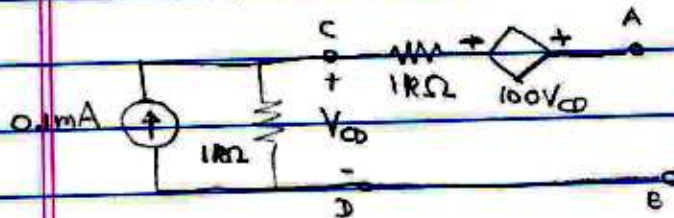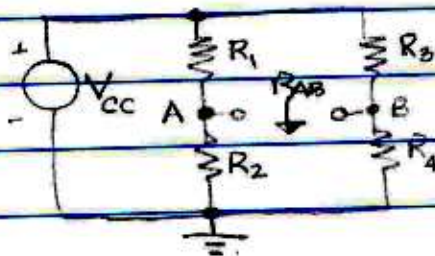


Obtain the Thevenin equivalent at terminals A-B.

PROBLEM 3

A) Find the condition for which $V_{AB} = 0$ B) If $R_1 = 4\Omega$, $R_2 = 12\Omega$, $R_3 = 2\Omega$, $R_4 = 6\Omega$
Evaluate R_{AB} .

PROBLEM 4

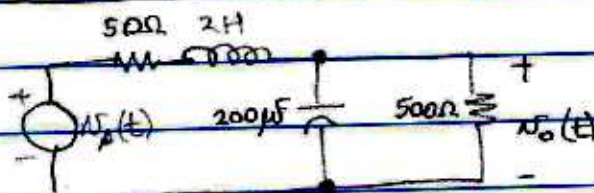

$$v_i(t) = 77 + 100 \cos 754t$$


A) Evaluate the steady-state response $v_o(t)$.

B) Derive the transfer function

$$H(j\omega) = V_o/V_i$$

C) Use the result in (B) to verify the result in (A).


PROBLEM 5

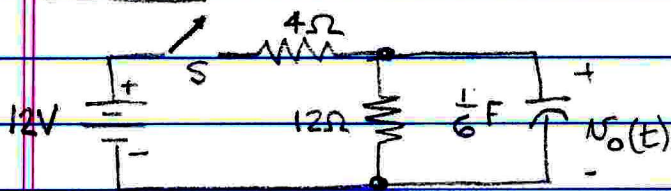

The switch S has been open for a long time and is closed at $t = 0$.

Evaluate $v_o(t)$ for $t \geq 0$.

PROBLEM 6

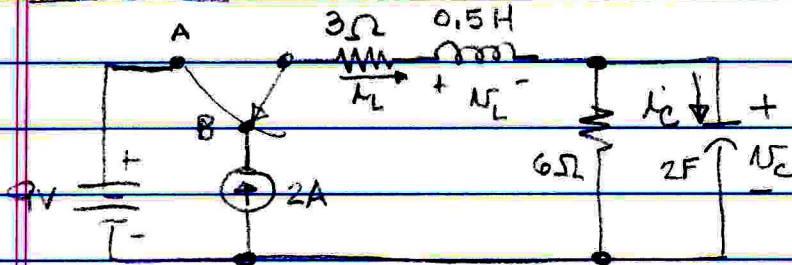

The switch S has been in position B for a long time. At $t = 0$ S is moved to position A .


Determine the following:

A) $i_L(0^+)$, $i_c(0^+)$, $v_L(0^+)$, $v_c(0^+)$

B) $i_L(\infty)$, $v_c(\infty)$.

PROBLEM 1


To calculate the resistance at a pair of terminals, apply a source (current/voltage) and measure the response (voltage/current) at the terminal pair. Then, $R = V/I$. In this problem a current source is applied as shown

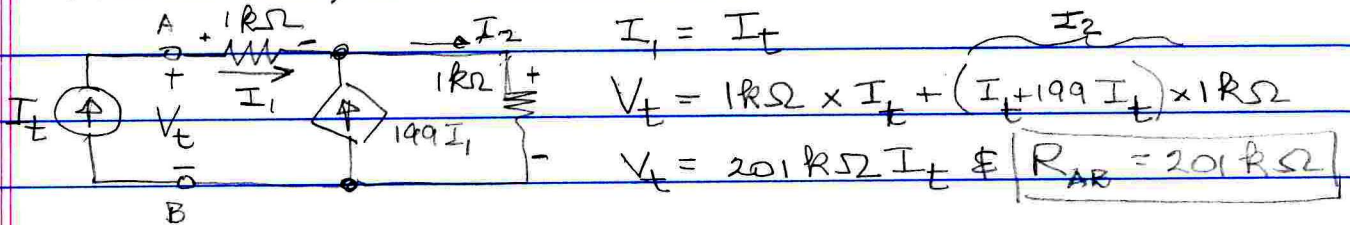

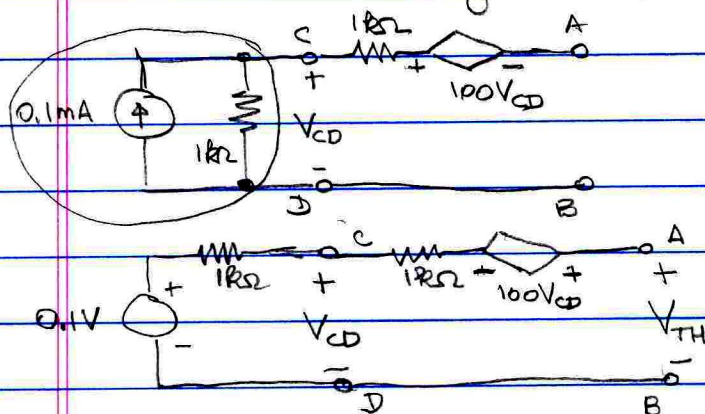PROBLEM 2

To obtain a Thévenin equivalent we must evaluate 2 of the following: V_{TH} , the open-circuit voltage; I_{SC} , the short-circuit current; R_{TH} , the resistance seen at the terminals in question. In this example, V_{TH} and I_{SC} will be evaluated, with $R_{TH} = V_{TH}/I_{SC}$.

WARNING: With a controlled source in the circuit, in general, one cannot use series/parallel reductions to get R_{TH}



Convert the encircled $0.1mA$ current source in parallel with $1k\Omega$ to its voltage source equivalent

No current exists so


$$V_{TH} = +100V_{CD} + 0.1$$

$$V_{CD} = 0.1 \text{ so } V_{TH} = +100 \times 0.1 + 0.1$$

$$V_{TH} = 10.1V$$

PROBLEM 2 (continued)

To obtain I_{sc} , short terminals A-B as shown

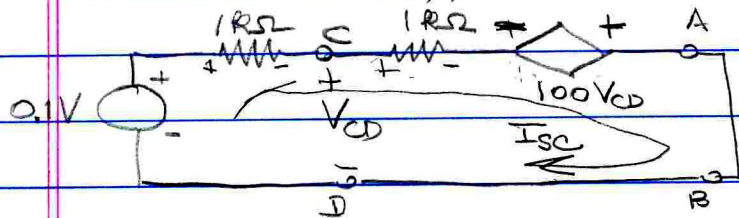KVL μ

$$(1) -0.1 + I_{sc} \times 1 + I_{sc} \times 1 - 100V_{CD} = 0$$

where I_{sc} is in mA

$$(1 \text{ mA} \times 1 \text{ k}\Omega = 1 \text{ V})$$

$$(2) V_{CD} = -1 \cdot I_{sc} + 0.1$$

Substitute (2) into (1) and solve for I_{sc} which yields

$$I_{sc} = 10.1/102, \quad R_{TH} = V_{TH}/I_{sc} = 10.1/(10.1/102) \quad \& \quad \boxed{R_{TH} = 102 \Omega}$$

PROBLEM 3

A) The balance condition for the Wheatstone bridge is obtained by calculation V_A and V_B with respect to ground. Each is a simple voltage divider.

$$V_A = \frac{R_2}{R_1 + R_2} V_{CC} \quad V_B = \frac{R_4}{R_3 + R_4} V_{CC}$$


$$V_{AB} = V_A - V_B = V_{CC} \left[\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right] = V_{CC} \left[\frac{R_2(R_3 + R_4) - R_4(R_1 + R_2)}{(R_1 + R_2)(R_3 + R_4)} \right]$$

$$V_{AB} = V_{CC} \left[\frac{R_2 R_3 - R_1 R_4}{(R_1 + R_2)(R_3 + R_4)} \right]$$

$$V_{AB} = 0 \text{ when } R_2 R_3 - R_1 R_4 = 0$$

$$\text{or } R_2 R_3 = R_1 R_4 \text{ or } \boxed{\frac{R_1}{R_2} = \frac{R_3}{R_4}}$$

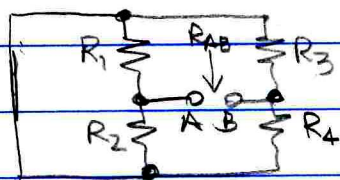B) To calculate R_{AB} we must suppress the independent source in the circuit. Thus,




Note R_1 is in parallel with R_2 and R_3 is in parallel with R_4 . These combinations are in series so

$$\boxed{R_{AB} = (R_1 \parallel R_2) + (R_3 \parallel R_4)}$$

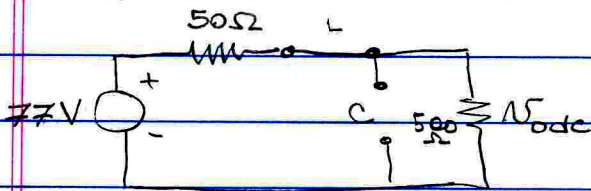PROBLEM 4

With two excitations, one dc and one ac, we must use superposition. For the dc excitation, the circuit is




Recall that in the dc steady-state inductances are short circuits and capacitances are open circuits

The circuit is a simple voltage divider so

$$V_{0dc} = \frac{500}{50 + 500} \times 77 \text{ and } V_{0dc} = 70 \text{ V}$$

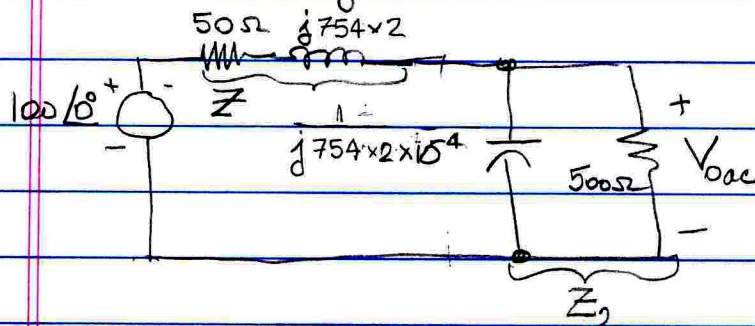For the ac circuit we use phasor analysis in which L becomes $j\omega L$ and C becomes $1/j\omega C$. The circuit is



$$Z_1 = 50 + j1508$$

$$Z_2 = 500 \parallel \left(\frac{1}{j754 \times 2 \times 10^{-4}} \right)$$


$$Z_2 = 500 \parallel -j6.33 = 6.63 \angle -89.24^\circ = 0.088 - j$$

$$V_{0ac} = \frac{6.63 \angle -89.24^\circ \times 100}{50 + j1508 + 0.088 - j6.63} = \frac{663 \angle -89.24^\circ}{1502 \angle 88.09^\circ} = 0.441 \angle -177.3^\circ$$

$$\therefore V_{0ac} = 0.441 \cos(754t - 177.3^\circ)$$


$$V_0(t) = V_{0dc} + V_{0ac} = 70 + 0.441 \cos(754t - 177.3^\circ)$$

PROBLEM 5

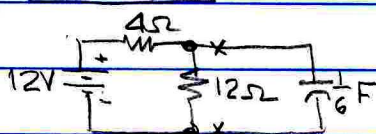

Circuit for $t \geq 0$

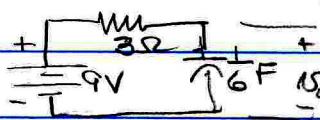Get Thévenin equivalent to the left of x-x



$$R_{TH} = 4 \parallel 12 = 3\Omega$$

$$V_{TH} = \frac{12}{12+4} \times 12 = 9 \text{ V}$$


We know V_0 starts at zero and charges to 9V with a time constant $= 3 \times \frac{1}{6} = \frac{1}{2}$

$$\therefore V_0(t) = 9(1 - e^{-t/2}) = 9(1 - e^{-0.5t})$$

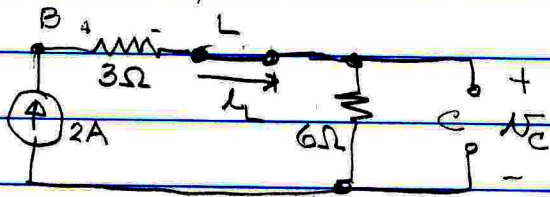PROBLEM 6


The key to this problem are the continuity relations for inductance current and capacitance voltage. These are that the current in an inductance and the voltage across a capacitance cannot change instantaneously. Thus, a change in excitation or circuit configuration at $t = T$ requires $i_L(T^+) = i_L(T^-)$ and $v_C(T^+) = v_C(T^-)$ where T^- is the instant before and T^+ is the instant just after the change occurs.

At $t = 0^-$, the circuit is in the dc steady state and is



Thus, $i_L(0^-) = 2A$ and $v_C(0^-) = 6 \times 2 = +12V$

At $t = 0^+$, the circuit becomes

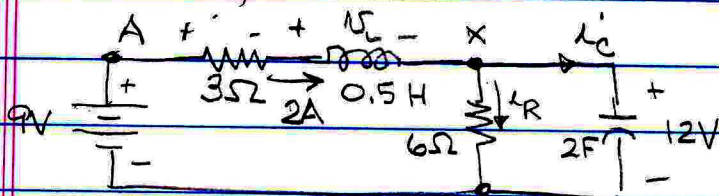

$$\boxed{i_L(0^+) = i_L(0^-) = 2A}$$

$$\boxed{v_C(0^+) = v_C(0^-) = 12V}$$

$i_R = 12/6 = 2$ and KCL @ X gives

$$-2 + i_R + i_C = 0 \text{ and } \boxed{i_C = 2 - 2 = 0}$$

KVL requires $-9 + 2 \times 3 + v_L + 12 = 0$ and $\boxed{v_L(0^+) = -9V}$