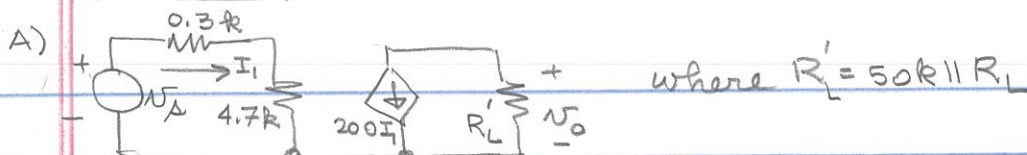


PROBLEM 1



$$I_1 = \frac{V_A}{0.3k + 4.7k} = \frac{V_A}{5k} \quad V_O = -200I_1 R'_L = -\frac{200 \times V_A}{5k} \times R'_L$$

$$|A_V| = -80 = \left| \frac{V_O}{V_A} \right| = \frac{200 R'_L}{5k} \quad \text{and } R'_L = \frac{80 \times 5k}{200} = 2k\Omega$$


$$R'_L = \frac{50 \times R_L}{50 + R_L} = 2 \quad (\text{all } R \text{ in } k\Omega)$$

Solving gives $48R_L = 100$ and $R_L = 2.083k\Omega$

B) For $A_V = 100$, I_1 remains the same but

$$V_O = -100 I_1 \times R'_L = -100 \times \frac{V_A}{5k} \times 2k \quad \text{and } |A_V| = 40$$

C) The circuit is

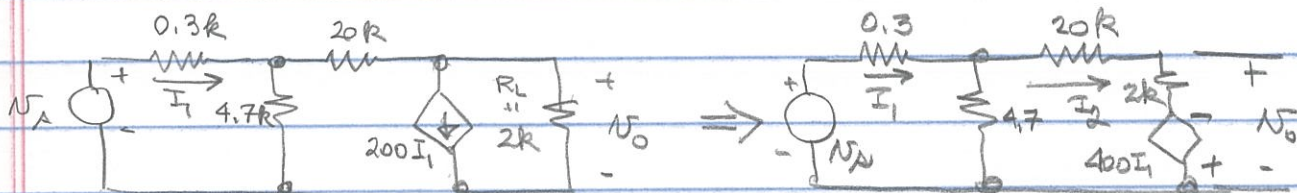

$$-V_A + I_1(0.3k) + 4.7(I_1 - I_2) = 0 \quad \text{or } 5k I_1 - 4.7k I_2 = V_A \quad (1)$$

$$4.7k(I_2 - I_1) + 20k I_2 + 2k I_2 + 400I_1 = 0 \quad \text{or } -404.7 I_1 + 26.7 I_2 = 0 \quad (2)$$

Solving (1) and (2) simultaneously gives

$$I_1 = -0.0151 V_A, \quad I_2 = -0.2288 V_A$$

$$\frac{V_O}{V_A} = 2 I_2 - 400 I_1 = 2(-0.2288) - 400(-0.0151) = 5.58$$

With $A_V = 100$, the equations are:


$$5k I_1 - 4.7k I_2 = V_A \quad (3); \quad -204.7 I_1 + 26.7 I_2 = 0$$

Simultaneous solution gives $I_1 = -0.03222 V_A$; $I_2 = -0.247 V_A$

$$V_O = -2(-0.247 V_A) - 200(-0.03222) V_A \quad \therefore \frac{V_O}{V_A} = 5.946$$

Note that the feedback reduced the gain but also reduced the variation. Also, it is allowed to use MATLAB.


PROBLEM 2

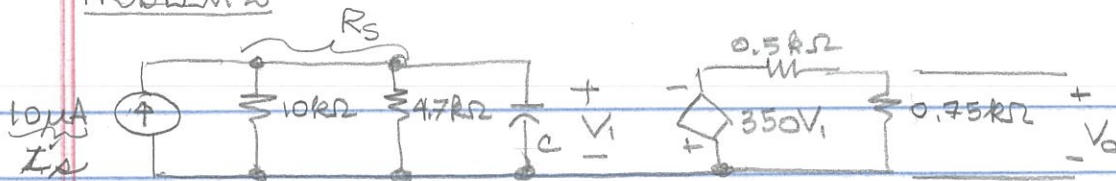

A) $C = 0$ (open-circuited); $10\text{ k}\Omega \parallel 4.7\text{ k}\Omega = R_S = \frac{10 \times 4.7}{10 + 4.7} = 3.2\text{ k}\Omega$
 $V_1 = 10\text{ }\mu\text{A} \times 3.2\text{ k}\Omega = 32\text{ mV}$; $V_0 = \frac{0.75}{0.75 + 0.5} \times (-350V_1) = 0.6(-350V_1) = -210V_1$
 $\therefore V_0 = -210 \times 32\text{ mV} = -6.72\text{ V}$

$$\frac{V_0}{I_A} = \frac{-6.72}{10^{-5}} = -6.72 \times 10^5 = -672 \times 10^3 = -672\text{ k}\Omega \left(\frac{\text{V}}{\text{A}} = \text{ohms} \right)$$

B) With C connected

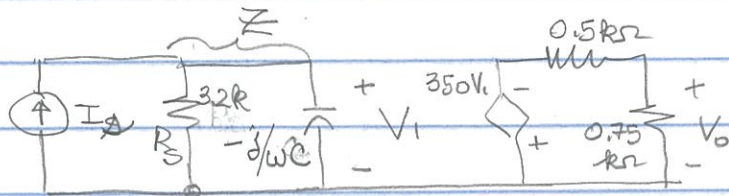

NOTE: The right-hand loop is independent of frequency. Thus,

the only cause of attenuation in V_0/I_A is due to C in the left hand loop. Therefore we must find out what value of C causes $|V_1(j2\pi \times 10^4)| = \frac{1}{\sqrt{2}} \times V_1$ (part A) given ω

$$V_1(j\omega) = I_A \times Z; \quad Z = R_S \parallel -j/\omega C = \frac{-jR_S/\omega C}{R_S - j/\omega C} \times \frac{j/\omega C}{j/\omega C}$$


$$I_A Z = \frac{R_S I_A}{1 + j\omega R_S C} = \frac{3.2 \times 10^3 \times 10^{-5}}{1 + j2\pi \times 10^4 \times 3.2 \times 10^3 C} = V_1 = \frac{3.2 \times 10^{-2}}{1 + j20.1 C \times 10^7}$$

$$|V_1| = \frac{3.2 \times 10^{-2}}{\sqrt{1 + (20.1 C \times 10^7)^2}} = \frac{3.2 \times 10^{-3}}{\sqrt{2}}$$

$$\text{or } 1 + (20.1 \times 10^7 C)^2 = 2 \quad \text{and } (20.1 \times 10^7 C)^2 = 1$$

$$\text{and } 20.1 \times 10^7 C = 1 \quad \text{or } C = 4.975 \times 10^{-9} \approx 4.98\text{ nF}$$

c) The circuit is

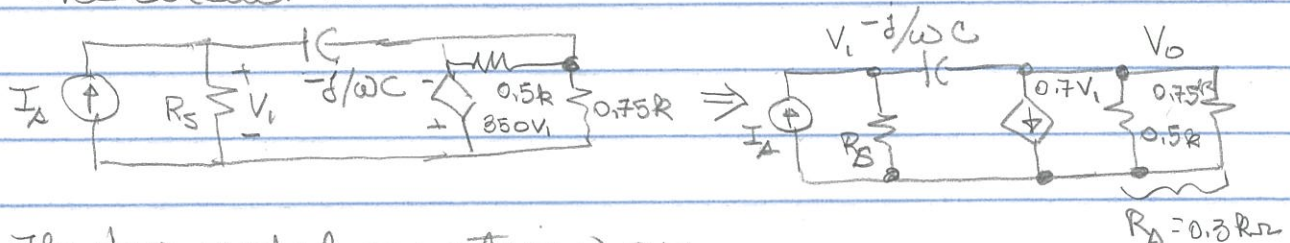

The two nodal equations are

$$R_A = 0.3\text{ k}\Omega$$

$$-I_A + \frac{V_1}{R_S} + \frac{V_1 - V_0}{-j\omega C} = 0 \quad \text{or} \quad V_1 \left(\frac{1}{R_S} + j\omega C \right) - j\omega C V_0 = I_A$$

$$+ \frac{(V_0 - V_1)}{-j\omega C} + \frac{V_0}{R_A} + 0.7V_1 = 0 \quad \text{or} \quad V_1 (0.7 - j\omega C) + V_0 \left(\frac{1}{R_A} + j\omega C \right) = 0$$

Solving for V_0 gives

$$V_0 = \frac{\begin{vmatrix} \frac{1}{R_S} + j\omega C & I_A \\ 0.7 - j\omega C & 0 \end{vmatrix}}{\begin{vmatrix} \frac{1}{R_S} + j\omega C & -j\omega C \\ 0.7 - j\omega C & \frac{1}{R_A} + j\omega C \end{vmatrix}} = \frac{-I_A (0.7 - j\omega C)}{\frac{1}{R_S R_A} - \omega^2 C^2 + \omega^2 C^2 + j\omega C \left[\frac{1}{R_A} + \frac{1}{R_S} + 0.7 \right]}$$

$$\frac{V_0}{I_A} = \frac{0.7 - j\omega C}{\frac{1}{3.2 \times 10^3 \times 0.3 \times 10^3} + j\omega C \left[\frac{1}{3.2 \times 10^3} + \frac{1}{0.3 \times 10^3} + 0.7 \right]}$$

$$\text{Evaluating gives } \frac{V_0}{I_A} = \frac{672 \times 10^3 (1 - j2\pi \times 10^4 \times 1.43)}{1 + j\omega C [0.3 \times 10^3 + 3.2 \times 10^3 + 0.7 \times 0.96 \times 10^6]}$$

The numerator term occurs well after the denominator term

$$\text{so } \omega C [3.5 \times 10^3 + 672 \times 10^3] = 1 \quad \text{or} \quad C = \frac{1}{2\pi \times 10^4 \times 672 \times 10^3}$$

$$\text{and } C = 23.7 \text{ pF}$$

NOTE: this value of C is 21 times smaller than in B.


D) The transfer function is

$$\frac{V_0}{I_A} = \frac{672 \times 10^3}{1 + j\omega / 2\pi \times 10^4} \quad \text{or} \quad \frac{672 \times 10^3}{1 + jf / 10^4}$$


$$\text{E) } f = 10^6, \quad \frac{V_0}{I_A} = \frac{672 \times 10^3}{1 + j10^6 / 10^4} = 672 \times 10^3 \text{ (magnitude)}$$

$$\text{For } \omega = 10^6, \quad \frac{V_0}{I_A} = \frac{672 \times 10^3}{1 + j10^6 / 2\pi \times 10^4} = \frac{672 \times 10^3}{1 + j15.9} \quad \text{and} \quad \left| \frac{V_0}{I_A} \right| = 42.1 \times 10^3$$

PROBLEM 3

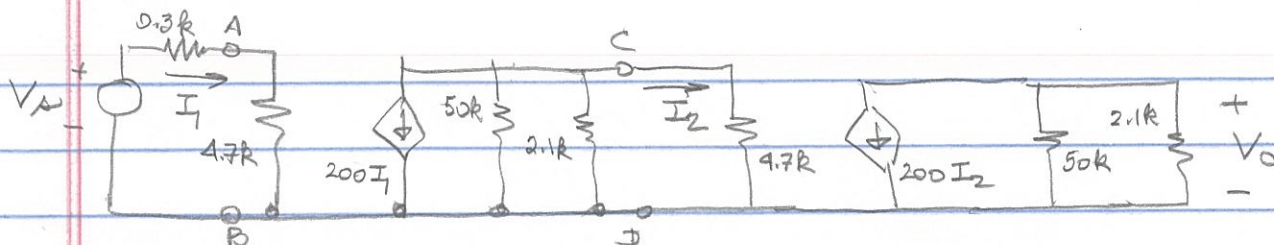

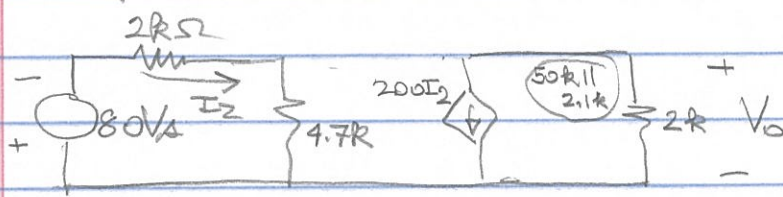- A) To the left of terminals c-b we have the circuit you analyzed in Problem 1. The Thévenin voltage $V_{TH} = -80V_A$ and the Thévenin resistance $R_{TH} = 50k \parallel 2.1k = 2k\Omega$. Then, the circuit becomes




$$I_2 = \frac{-80V_A}{\underbrace{2k + 4.7k}_{6.7k}}$$

$$V_O = -200 \times \left(\frac{-80V_A}{6.7k\Omega} \right) \times 2k = 4,776V_A$$

$$G_{\text{new}} = \frac{V_O}{V_A} = 4,776$$

- B) No, it is lower. Even though the circuits look alike they differ in one significant way. Stage 1 has a source resistance of $0.3k\Omega$ while Stage 2 is driven by $R_{TH} = 2k\Omega$. Thus, in the left hand loop $R_{\text{TOTAL}} = 5k\Omega$ for Stage 1 and $6.7k\Omega$ for Stage 2. Their ratio is 1.34 just the amount that the overall gain deviates from 6,400.

2.12 Text

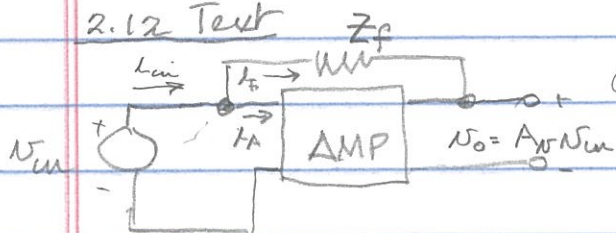

a) $Z_{in} = V_{in} / I_{in}$; $I_{in} = I_f$
 $I_f = \frac{V_{in} - A_v V_{in}}{Z_f}$ or $Z_{f, in} = V_{in} (1 - A)$
 $\therefore Z_{in} = Z_f / (1 - A)$

$$b) Z_{in} = \frac{10k\Omega}{1 - (-10^5)} = 0.1\Omega$$

$$c) Z_{in} = \frac{10k\Omega}{1 - 2} = -10k\Omega$$

Circuit uses positive feedback and will oscillate prior to measurement. The circuit is unstable and once the amplifier's frequency response is included, it will oscillate.

$$d) Z_{in} = \frac{-j/\omega C}{1 - (-100)} = \frac{-j}{\omega C(101)} = \frac{-j}{\omega \times 101 \times 10^{-12}}$$

Input looks like a 101 pF capacitor. This is used extensively in IC design to limit the area required to fabricate a "large" capacitor. In the 741 Op-Amp a $C = 30pF$ is used to obtain a -3dB frequency of 5Hz. The effective resistance is $1M\Omega$

$$5 = \frac{1}{2\pi 10^6 C} \text{ or } C \approx 31.5nF$$

With a gain (A_v) of just over 1,000 this C becomes the needed 31.5nF