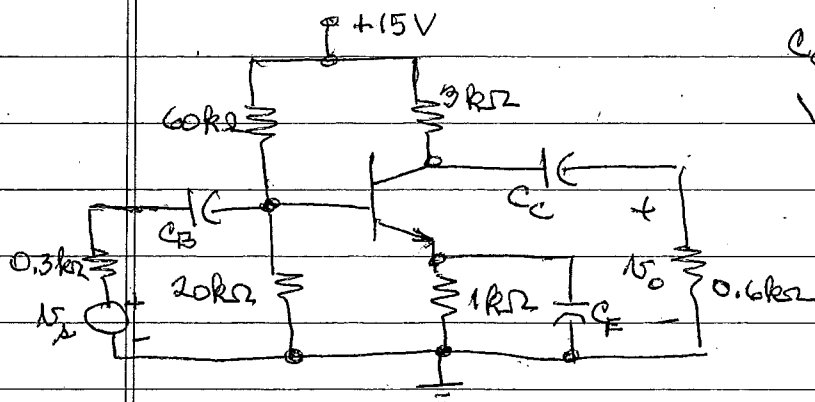
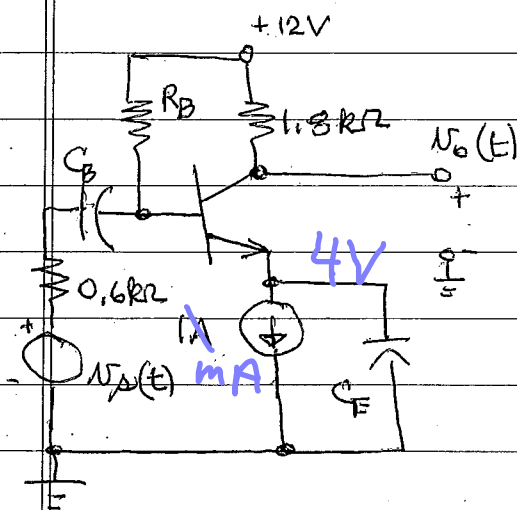


NOTES: 1) Both HW #5 and #6 are due on Thursday March 17.
 2) In all problems $V_T = 25\text{mV}$ and $v_{in}(t) = 50 \sin \omega t \text{ mV}$.

PROBLEM I:

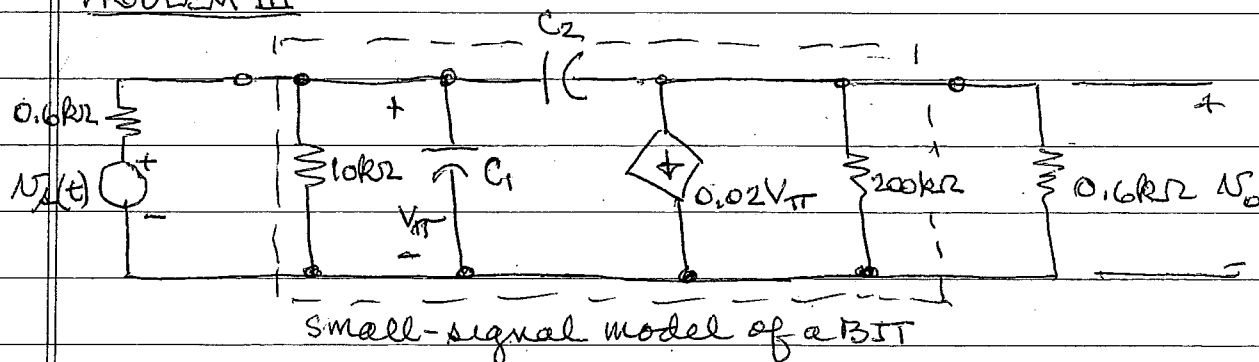
C_C, C_B and C_E are all infinite
 $V_A \rightarrow \infty, \beta = 200$
 Determine $A_v = \frac{v_o}{v_{in}}$

PROBLEM II

$\beta = 100, V_A \rightarrow \infty$

A) Determine R_B

B) Evaluate $v_o(t)$.

PROBLEM III

A) With $C_2 = 0$, determine C_1 to obtain a high-frequency 3dB frequency of 40MHz.

B) With $C_1 = 0$, determine C_2 to obtain a 40MHz 3dB frequency.