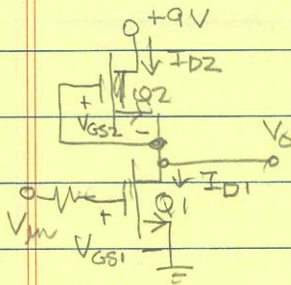


PROBLEM A



Observations: $I_{D1} = I_{D2}$, $V_{DS1} + V_{DS2} = V_{DD}$

$$V_{GS1} = V_{in}; V_{GS2} = 0, V_{DS1} = V_0$$


Based on the characteristics, for $V_{in} \leq 2V$, where $V_{t1} = 2V$, $Q1$ is cutoff so $I_{D1} = 0$

Thus, $I_{D2} = 0$. On the $Q2$ characteristics, for $V_{GS2} = 0$, the only place $I_{D2} = 0$ is the origin. Then $V_{DS2} = 0$


and $V_{DS1} = V_{DD}$. As V_{in} increases slightly above $2V$, $Q1$ begins to conduct slightly but is still less than $800\mu A$. Thus, $Q2$ operates "near" the origin and V_{DS2} is small so $V_{DS1} = V_0 =$ a bit less than V_{DD} .

When $V_{in} > 4V$, $Q1$ is capable of conducting at $> 800\mu A$. However, $Q2$ limits the current to $800\mu A$ and V_{DS1} becomes "small" and V_{DS2} begins to approach V_{DD} . This process continues as V_{in} increases beyond $4V$.

The transfer characteristic is

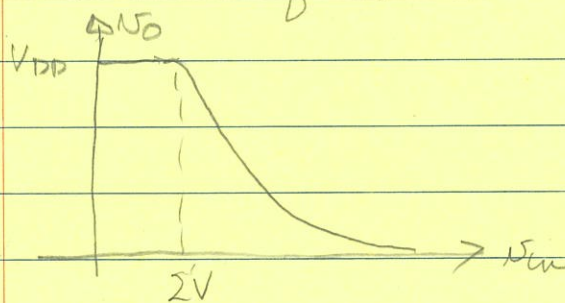


PROBLEM B

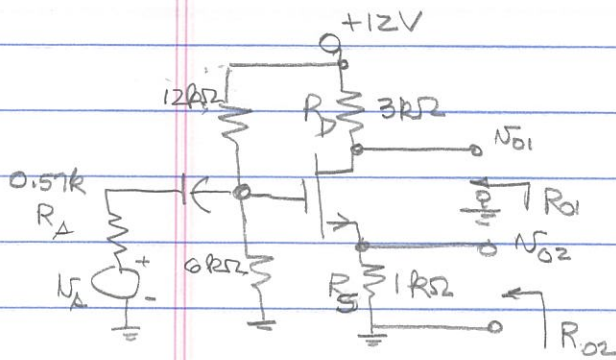


$$I_D = 0.8 (V_{GS} - 2)^2 \text{ mA} \quad V_A = 60 \text{ k}\Omega$$

The dc circuit is

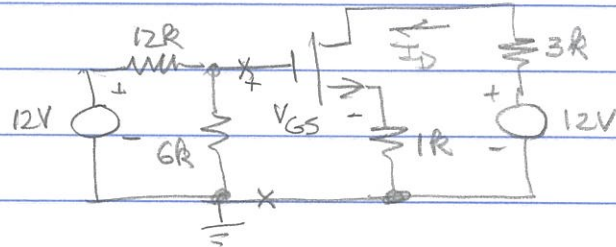

Get Thevenin equivalent to the left of X-X.
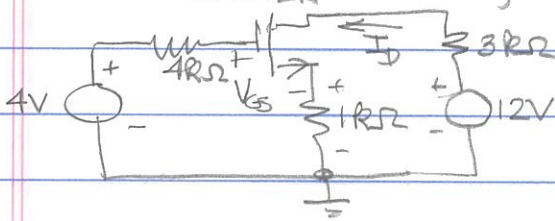
$$V_{TH} = \frac{6k}{6k+12k} \times 12 = 4V, \quad R_{TH} = 6k \parallel 12k = 4k\Omega$$



$$V_{GS} = 4 - 1k \times I_D \text{ (mA)} = 4 - 1 \cdot I_D$$

Substitute this for V_{GS} in I_D equation and get

$$0.8 (4 - I_D - 2)^2 = I_D \quad \text{all currents in mA}$$

$$0.8 (2 - I_D)^2 = I_D \quad \text{or} \quad 0.8 (4 - 4I_D + I_D^2) = I_D$$

$$\text{and } 4 - 4I_D + I_D^2 = 1.25 I_D \quad \text{and } I_D^2 - 5.25 I_D + 4 = 0$$

$$I_D = \frac{5.25 \pm \sqrt{(5.25)^2 - 16}}{2} \quad \text{and } I_D = 0.925 \text{ mA}; \quad \text{or } I_D = 4.325 \text{ mA}$$

$I_D = 4.325 \text{ mA}$ is not physically possible as $3 \times 4.325 = 12.975$ which is higher than the supply voltage. Also,

$$I_D \times 1k = 4.325 \text{ V makes } V_{GS} = 4 - 4.325 = -0.325 \text{ V,}$$

well below the threshold voltage putting the MOSFET off! Must select $I_D = 0.925 \text{ mA}$


KVL for the drain loop is

$$-12 + I_D \times 3k + V_{CE} + I_D \times 1k = 0 \quad \text{or } V_{CE} = 12 - 4I_D$$


$$V_{CE} = 12 - 4 \times 0.925 = 8.3 \text{ V}$$

PROBLEM C

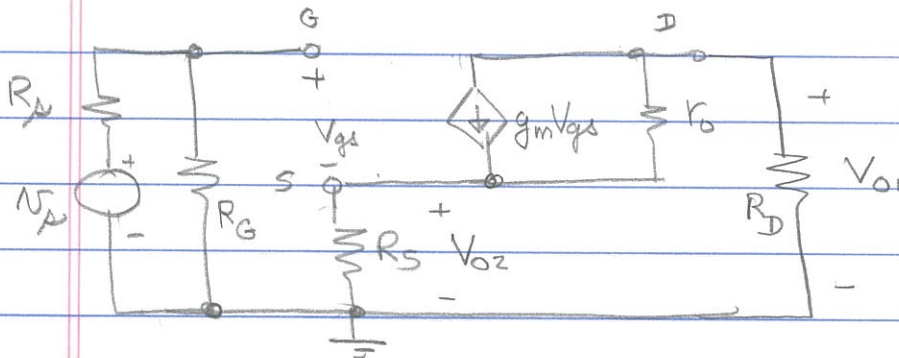1. The small-signal model of the common-source stage in Prob. B is



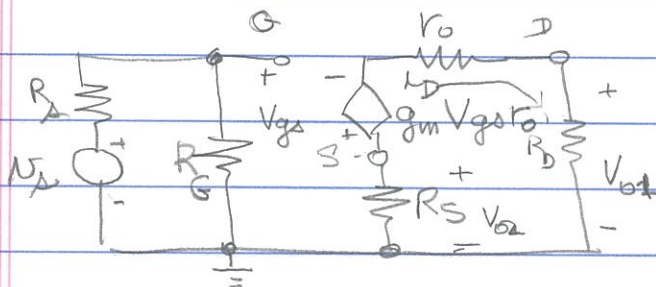Best way to proceed is to convert $g_m V_{GS}$ in parallel with r_o to its voltage-source series R .



$$V_{GS} = V_G - V_S$$

$$V_G = \frac{R_G}{R_G + R_A} V_A$$

$$V_S = -I_D R_S$$

$$V_{GS} = \frac{R_G V_A}{R_G + R_A} + I_D R_S = \alpha V_A + I_D R_S$$

KVL Drain loop: $r_o g_m V_{GS} + I_D (r_o + R_D + R_S) = 0$ and

$$-r_o g_m \alpha V_A + I_D [r_o + R_D + R_S (1 + g_m r_o)] = 0$$

$$I_D = \frac{-g_m r_o \alpha V_A}{r_o + R_D + R_S (1 + g_m r_o)}$$

$$V_{O1} = -I_D R_D = \frac{-g_m r_o \alpha R_D V_A}{r_o + R_D + R_S (1 + g_m r_o)}$$

$$V_{O2} = I_D R_S = \frac{g_m r_o \alpha V_A R_S}{r_o + R_D + R_S (1 + g_m r_o)}$$

These are the literal answers to (4) and (5)
(6) and (7) are both yes.

2. $A_{V1} = \left. \frac{V_{O1}}{V_A} \right|_{R_S=0} = \frac{-g_m r_o \alpha R_D}{r_o + R_D}$ 3. $A_{V2} = \left. \frac{V_{O2}}{V_A} \right|_{R_D=0} = \frac{g_m r_o \alpha R_S}{r_o + R_S (1 + g_m r_o)}$

The numerical answers to Problem C use

$$g_m = 2\sqrt{K I_{DQ}} = 2\sqrt{0.8 \times 0.925} = \underbrace{1.72}_{\text{mA/V}^2}; \quad r_o = 60 \text{ k}\Omega$$

$$\alpha = \frac{R_G}{R_G + R_A} = \frac{4 \text{ k}}{4 \text{ k} + 0.57 \text{ k}} = 0.875$$

$$2) \quad A_{V1} = \frac{-1.72 \times 60 \times 0.875 \times 3}{60 + 3 + 1(1 + 1.72 \times 60)} = -4.3$$

$$3) \quad A_{V2} = \frac{1.72 \times 60 \times 0.875 \times 1}{60 + 1(1 + 1.72 \times 60)} = 0.55$$

$$4) \quad A_{V3} = \frac{-1.72 \times 60 \times 0.875 \times 3}{60 + 3 + 1(1 + 1.72 \times 60)} = -1.62$$

$$5) \quad A_{V4} = \frac{1.72 \times 60 \times 0.875 \times 1}{60 + 3 + 1(1 + 1.72 \times 60)} = 0.54$$

PROBLEM D

To obtain R_{O1} and R_{O2} we can use Thévenin's theorem. The Thévenin resistance is V_{TH}/I_{SC} . We already have V_{TH} for both. To obtain I_{SC} , make $R_D = 0$ and find $I_D|_{R_D=0}$ to get R_{O1} ; for R_{O2} make $R_S = 0$ and get $I_D|_{R_S=0}$. Then take the appropriate ratio!

$$V_{TH1} = -g_m r_o \alpha R_D V_A / [r_o + R_D + R_S(1 + g_m r_o)]$$

$$I_D|_{R_D=0} = -g_m r_o \alpha V_A / [r_o + R_S(1 + g_m r_o)]$$

$$R_{O1} = V_{TH1} / I_D|_{R_D=0} = R_D [r_o + R_S(1 + g_m r_o)] / [r_o + R_D + R_S(1 + g_m r_o)]$$

$$\text{This is simply } R_D \parallel [r_o + R_S(1 + g_m r_o)]$$

$$V_{TH2} = g_m r_o \alpha R_S V_A / [r_o + R_D + R_S(1 + g_m r_o)]$$

$$I_D|_{R_S=0} = g_m r_o \alpha V_A / [r_o + R_D]$$

$$R_{O2} = V_{TH2} / I_D|_{R_S=0} = R_S (r_o + R_D) / [r_o + R_D + R_S(1 + g_m r_o)]$$

Rewriting R_{o2} as

$$R_{o2} = \frac{R_S(r_o + R_D)}{r_o + R_D + R_S + g_m r_o R_S} = \frac{R_S(r_o + R_D)}{r_o + R_D + R_S} \times \frac{1}{1 + \frac{g_m r_o R_S}{r_o + R_D + R_S}}$$

The first term is $R_S \parallel (r_o + R_D)$ and the second illustrates the impedance reduction of the feedback provided by R_S . Note that R_D is part of the input loop affecting V_{gs} and R_S is part of the output loop indicating feedback.

Numerically, the values are

$$R_{o1} = 3 \parallel [60 + 3 + 1(1 + 1.72 \times 60)] = 3 \parallel 167.2 = 2.95 \text{ k}\Omega$$

$$R_{o2} = [1 \parallel (60 + 3)] \times \frac{1}{1 + \frac{1.72 \times 60 \times 1}{60 + 3 + 1}} = 0.984 \times \frac{1}{2.61} = 0.376 \text{ k}\Omega$$

Observe: For R_{o1} , the effect of the feedback makes the term in the $[\]$ larger so that the parallel combination is more closely $3 \text{ k}\Omega = R_D$. For R_{o2} , the effect of feedback reduces the output resistance. The resistance seen by R_D in R_{o1} increases because of the feedback provided by R_S .